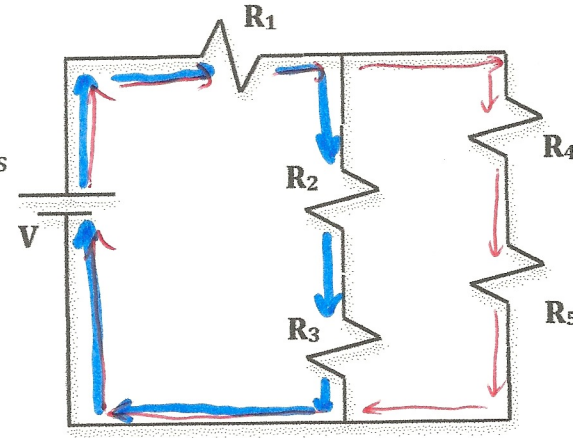


Example 13:


Five resistors are connected to an 18.0 v battery. The resistors have values as follows:

- $R_1 = 90.0 \Omega$
- $R_2 = 60.0 \Omega$
- $R_3 = 45.0 \Omega$
- $R_4 = 10.0 \Omega$
- $R_5 = 35.0 \Omega$

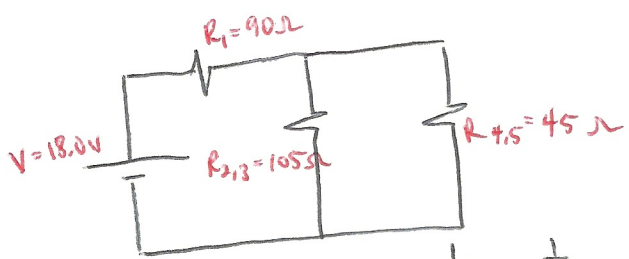
- A. What is the equivalent resistance?
- B. What is the current at the battery?
- C. What is the current and voltage drop through each resistor?



$R_{2,3} = R_2 + R_3 = 60 + 45 = 105 \Omega$
 $R_{4,5} = R_4 + R_5 = 10 + 35 = 45 \Omega$



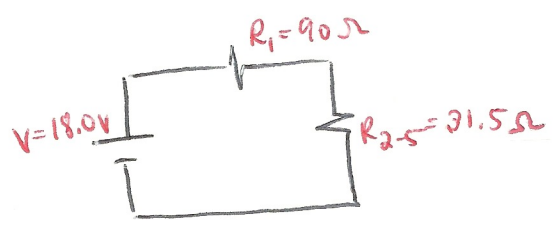$\frac{1}{R_{2-5}} = \frac{1}{R_{2,3}} + \frac{1}{R_{4,5}} = \frac{1}{105} + \frac{1}{45}$
 $\frac{1}{R_{2-5}} = 0.0317$
 $R_{2-5} = 31.5 \Omega$



$R_{eq} = R_1 + R_{2-5} = 90 + 31.5$
 $R_{eq} = 121.5 \Omega \approx 122 \Omega$

