

Honors Physics: Circuits
Class Examples


Combination Circuits

Example 12

A series and parallel circuit combination has a voltage of 18.0 v at the source. The values of the resistors are as follows:

- $R_1 = 53.00 \Omega$ $R_3 = 95.00 \Omega$
 $R_2 = 65.00 \Omega$ $R_4 = 75.00 \Omega$

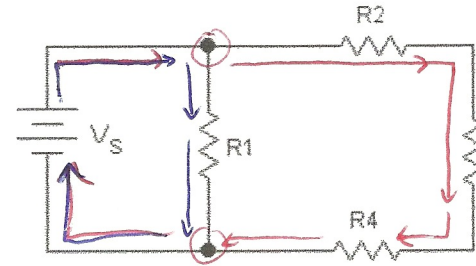
- A. Find the equivalent resistance (R_{eq})
B. Find the total current at the battery.
C. Find the current and voltage drop across each resistor.



$$R_{2,3,4} = R_2 + R_3 + R_4$$

$$R_{2,3,4} = 65 + 95 + 75$$

$$R_{2,3,4} = 235 \Omega$$

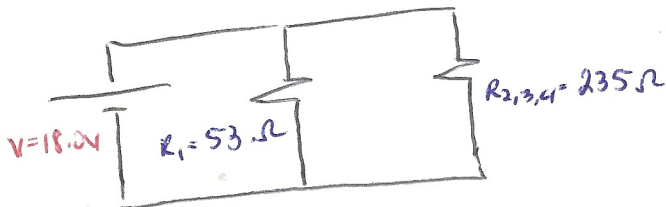


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_{2,3,4}}$$

$$\frac{1}{R_{eq}} = \frac{1}{53} + \frac{1}{235}$$

$$\frac{1}{R_{eq}} = 0.0231$$

$$R_{eq} = 43.2 \Omega$$

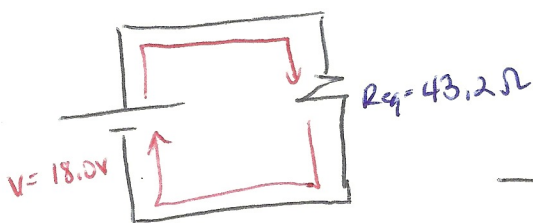

$$V = I \cdot R$$

$$I = \frac{V}{R} = \frac{18}{43.2}$$

$$I = 0.417 \text{ A}$$

