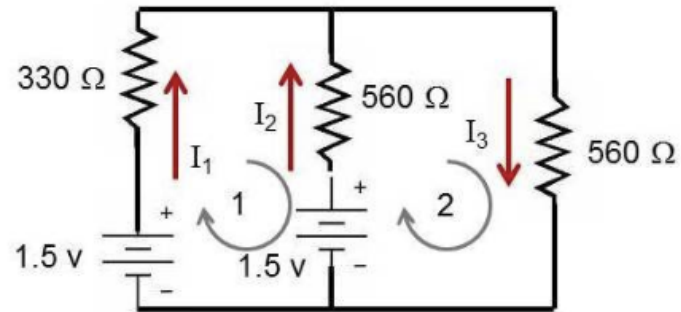


Name: _____

AP Physics 1: DC Circuits
Kirchhoff's Laws HW

Use the image below to identify all currents in the circuit.

Circuit 1



Circuit 2

